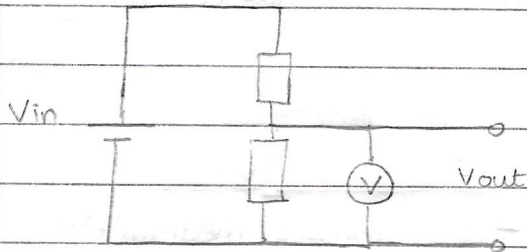


* Practical Circuits *

Q-1) Potential dividers.




$$V_{out} = \left(\frac{R_2}{R_1 + R_2} \right) \times V_{in}$$

↓
total voltage flowing across
the 2 resistors.

Q-2) Potentiometer

> used for :

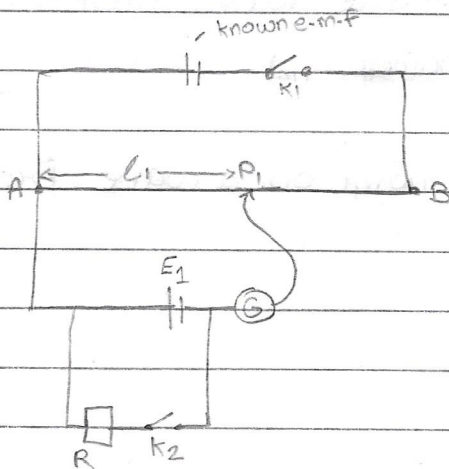- ① measuring e.m.f of a cell
- ② comparing e.m.f's of 2 cells
- ③ finding internal resistance of a cell



- ① the key K_1 is closed and the null point P_1 is found (zero deflection on galvanometer) the distance from A to P_1 is l_1 .

$$\Rightarrow E_1 \propto l_1$$

- ② Both keys, K_1 and K_2 are closed and the new null point P_2 is found. the distance from A to P_2 is l_2 .

$$\Rightarrow V \propto l_2$$

$$\frac{E_1}{V} = \frac{l_1}{l_2}$$

$$E_1 = I(R+x) \\ V = IR$$

$$\therefore \frac{I(R+x)}{IR} = \frac{l_1}{l_2}$$

$$\therefore x = \frac{R(l_1 - l_2)}{l_2}$$